

Computer Architecture - Project 1A

Datapath Design

Vsevolod Syrtsov

`syrtsov@tcd.ie`

source: github.com/futurecertificate

Lecturer: Dr. Michael Manzke

Contents

1	VHDL Sources	2
1.1	16 bit Register	2
1.2	Decoder 3 to 8	2
1.3	Multiplexer 2 to 16	3
1.4	Multiplexer 8 to 16	4
1.5	Register File	4
2	Component Test Benches	10
2.1	Register Testbench	10
2.2	Decoder 3 to 8	11
2.3	Multiplexer 2 to 16	14
2.4	Multiplexer 8 to 16	16
2.5	Register File	18
3	Testbench Results	22
3.1	Register	22
3.2	Decoder	22
3.3	2-16 Multiplexer	23
3.4	8-16 Multiplexer	23
3.5	Register File	23

1 VHDL Sources

1.1 16 bit Register

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity reg16 is
port (
D : in std_logic_vector(15 downto 0);
load, Clk : in std_logic;
Q : out std_logic_vector(15 downto 0)
);

end reg16;
architecture Behavioral of reg16 is
begin
process(Clk)
begin
if (rising_edge(Clk)) then
if load='1' then
Q<=D after 5 ns;
end if;
end if;
end process;
end Behavioral;
```

1.2 Decoder 3 to 8

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity decoder3_8 is
Port ( A0 : in std_logic;
A1 : in std_logic;
A2 : in std_logic;

Q0 : out std_logic;
Q1 : out std_logic;
```

```

Q2 : out std_logic;
Q3 : out std_logic;
Q4 : out std_logic;
Q5 : out std_logic;
Q6 : out std_logic;
Q7 : out std_logic);

end decoder3_8;
architecture Behavioral of decoder3_8 is
begin
Q0<= ((not A0) and (not A1) and (not A2)) after 5 ns;
Q1<= ((not A0) and (not A1) and A2) after 5 ns;
Q2<= ((not A0) and A1 and (not A2)) after 5 ns;
Q3<= ((not A0) and A1 and A2) after 5 ns;
Q4<= (A0 and (not A1) and (not A2)) after 5 ns;
Q5<= (A0 and (not A1) and A2) after 5 ns;
Q6<= (A0 and A1 and (not A2)) after 5 ns;
Q7<= (A0 and A1 and A2) after 5 ns;

end Behavioral;

```

1.3 Multiplexer 2 to 16

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity mux2_16 is
port (
In0 : in std_logic_vector(15 downto 0);
In1 : in std_logic_vector(15 downto 0);
s : in std_logic;
Z : out std_logic_vector(15 downto 0));

end mux2_16;
architecture Behavioral of mux2_16 is
begin
Z <= In0 after 5 ns when S='0' else
In1 after 5 ns when S='1' else
"0000000000000000" after 5 ns;

```

```
end Behavioral;
```

1.4 Multiplexer 8 to 16

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity mux8_16 is
Port ( In0, In1, In2, In3, In4, In5, In6, In7 : in std_logic_vector(15 downto 0)
S0, S1, S2 : in std_logic;
Z : out std_logic_vector(15 downto 0));

end mux8_16;
architecture Behavioral of mux8_16 is
begin
Z <= In0 after 5 ns when S0='0' and S1='0' and S2 ='0' else
In1 after 5 ns when S0='0' and S1='0' and S2 ='1' else
In2 after 5 ns when S0='0' and S1='1' and S2 ='0' else
In3 after 5 ns when S0='0' and S1='1' and S2 ='1' else
In4 after 5 ns when S0='1' and S1='0' and S2 ='0' else
In5 after 5 ns when S0='1' and S1='0' and S2 ='1' else
In6 after 5 ns when S0='1' and S1='1' and S2 ='1' else
In7 after 5 ns when S0='1' and S1='1' and S2 ='1' else
"0000000000000000" after 5 ns;
end Behavioral;
```

1.5 Register File

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity reg_file is
Port (
src_s0 : in std_logic;
src_s1 : in std_logic;
src_s2 : in std_logic;

des_A0 : in std_logic;
des_A1 : in std_logic;
```

```

des_A2 : in std_logic;

Clk : in std_logic;
data_src : in std_logic;

data : in std_logic_vector(15 downto 0);
reg0 : out std_logic_vector(15 downto 0);
reg1 : out std_logic_vector(15 downto 0);
reg2 : out std_logic_vector(15 downto 0);
reg3 : out std_logic_vector(15 downto 0);
reg4 : out std_logic_vector(15 downto 0);
reg5 : out std_logic_vector(15 downto 0);
reg6 : out std_logic_vector(15 downto 0);
reg7 : out std_logic_vector(15 downto 0)
);

end reg_file;

architecture Behavioral of reg_file is

COMPONENT reg16
PORT(

D : IN std_logic_vector(15 downto 0);
load : IN std_logic;
Clk : IN std_logic;
Q : OUT std_logic_vector(15 downto 0)
);

END COMPONENT;

COMPONENT mux8_16
PORT(

In0 : IN std_logic_vector(15 downto 0);
In1 : IN std_logic_vector(15 downto 0);
In2 : IN std_logic_vector(15 downto 0);
In3 : IN std_logic_vector(15 downto 0);
In4 : IN std_logic_vector(15 downto 0);
In5 : IN std_logic_vector(15 downto 0);
In6 : IN std_logic_vector(15 downto 0);

```

```
In7 : IN std_logic_vector(15 downto 0);
```

```
S0 : IN std_logic;
```

```
S1 : IN std_logic;
```

```
S2 : IN std_logic;
```

```
Z : OUT std_logic_vector(15 downto 0)
```

```
);
```

```
END COMPONENT;
```

```
COMPONENT mux2_16
```

```
PORT(
```

```
In0 : IN std_logic_vector(15 downto 0);
```

```
In1 : IN std_logic_vector(15 downto 0);
```

```
s : IN std_logic;
```

```
Z : OUT std_logic_vector(15 downto 0)
```

```
);
```

```
END COMPONENT;
```

```
COMPONENT decoder3_8
```

```
PORT(
```

```
A0 : IN std_logic;
```

```
A1 : IN std_logic;
```

```
A2 : IN std_logic;
```

```
Q0 : OUT std_logic;
```

```
Q1 : OUT std_logic;
```

```
Q2 : OUT std_logic;
```

```
Q3 : OUT std_logic;
```

```
Q4 : OUT std_logic;
```

```
Q5 : OUT std_logic;
```

```
Q6 : OUT std_logic;
```

```
Q7 : OUT std_logic
```

```
);
```

```
END COMPONENT;
```

```
signal load_reg0, load_reg1, load_reg2, load_reg3, load_reg4, load_reg5, load_reg6, load_reg7;
```

```
signal reg0_q, reg1_q, reg2_q, reg3_q, reg4_q, reg5_q, reg6_q, reg7_q, data_src_0, data_src_1, data_src_2, data_src_3, data_src_4, data_src_5, data_src_6, data_src_7;
```

```
begin
```

```

reg00: reg16 PORT MAP(

D => data_src_mux_out,
load => load_reg0,
Clk => Clk,
Q => reg0_q

);

reg01: reg16 PORT MAP(

D => data_src_mux_out,
load => load_reg1,
Clk => Clk,
Q => reg1_q

);

reg02: reg16 PORT MAP(

D => data_src_mux_out,
load => load_reg2,
Clk => Clk,
Q => reg2_q

);

reg03: reg16 PORT MAP(

D => data_src_mux_out,
load => load_reg3,
Clk => Clk,
Q => reg3_q

);

reg04: reg16 PORT MAP(

D => data_src_mux_out,
load => load_reg4,

```

```

Clk => Clk,
Q => reg4_q

);

reg05: reg16 PORT MAP(

D => data_src_mux_out,
load => load_reg5,
Clk => Clk,
Q => reg5_q

);

reg06: reg16 PORT MAP(

D => data_src_mux_out,
load => load_reg6,
Clk => Clk,
Q => reg6_q

);

reg07: reg16 PORT MAP(

D => data_src_mux_out,
load => load_reg7,
Clk => Clk,
Q => reg7_q

);

decoder_3_8: decoder3_8 PORT MAP(

A0 => des_A0,
A1 => des_A1,
A2 => des_A2,

Q0 => load_reg0,
Q1 => load_reg1,
Q2 => load_reg2,

```



```

Q3 => load_reg3,
Q4 => load_reg4,
Q5 => load_reg5,
Q6 => load_reg6,
Q7 => load_reg7

);

data_src_mux2_16bit: mux2_16 PORT MAP(

In0 => data,
In1 => src_reg,
s => data_src,
Z => data_src_mux_out

);

Inst_mux2_16bit: mux8_16 PORT MAP(

In0 => reg0_q,
In1 => reg1_q,
In2 => reg2_q,
In3 => reg3_q,
In4 => reg4_q,
In5 => reg5_q,
In6 => reg6_q,
In7 => reg7_q,

S0 => src_s0,
S1 => src_s1,
S2 => src_s2,
Z => src_reg

);

reg0 <= reg0_q;
reg1 <= reg1_q;
reg2 <= reg2_q;
reg3 <= reg3_q;
reg4 <= reg4_q;
reg5 <= reg5_q;
reg6 <= reg6_q;

```

```
reg7 <= reg7_q;

end Behavioral;
```

2 Component Test Benches

2.1 Register Testbench

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY tbreg16 IS
END tbreg16;

ARCHITECTURE behavior OF tbreg16 IS

    COMPONENT reg16
    PORT(
        D : IN  std_logic_vector(15 downto 0);
        load : IN  std_logic;
        clk : IN  std_logic;
        Q : OUT std_logic_vector(15 downto 0)
    );
    END COMPONENT;

    signal D : std_logic_vector(15 downto 0) := (others => '0');
    signal load : std_logic := '0';
    signal clk : std_logic := '0';

    signal Q : std_logic_vector(15 downto 0);

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: reg16 PORT MAP (
        D => D,
```

```

        load => load,
        clk => clk,
        Q => Q
    );

    -- Clock process definitions
    clk_process :process
    begin
        clk <= '0';
        wait for 5ns;
        clk <= '1';
        wait for 5ns;
    end process;

    -- Stimulus process
    stim_proc: process
    begin
        wait for 10ns;
        D <= x"1234";
        load <= '1';

        wait for 10ns;
        load <= '0';

        wait for 10ns;
        D <= x"FFFF";
        load <= '1';

        wait for 10ns;
        load <= '0';
    end process;

END;
```

2.2 Decoder 3 to 8

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity tb3_8dec is
```

```

end tb3_8dec;

architecture Behavioral of tb3_8dec is
COMPONENT decoder3_8
    PORT(
        A0 : IN  std_logic;
        A1 : IN  std_logic;
        A2 : IN  std_logic;

        Q0 : out  std_logic;
        Q1 : out  std_logic;
        Q2 : out  std_logic;
        Q3 : out  std_logic;
        Q4 : out  std_logic;
        Q5 : out  std_logic;
        Q6 : out  std_logic;
        Q7 : out  std_logic
    );
END COMPONENT;

    --Inputs

    signal A0 : std_logic := '0';
    signal A1 : std_logic := '0';
    signal A2 : std_logic := '0';

    --Outputs
    signal Q0 : std_logic;
    signal Q1 : std_logic;
    signal Q2 : std_logic;
    signal Q3 : std_logic;
    signal Q4 : std_logic;
    signal Q5 : std_logic;
    signal Q6 : std_logic;
    signal Q7 : std_logic;

begin
    --Unit Under Testing
    uut: decoder3_8 PORT MAP (
        Q0 => Q0,

```

```

        Q1 => Q1,
        Q2 => Q2,
        Q3 => Q3,
        Q4 => Q4,
        Q5 => Q5,
        Q6 => Q6,
        Q7 => Q7,

        A0 => A0,
        A1 => A1,
        A2 => A2

    );
stim_proc: process
begin
    wait for 10ns;
    A0 <= '0';
    A1 <= '0';
    A2 <= '0';

    wait for 10ns;
    A0 <= '0';
    A1 <= '0';
    A2 <= '1';

    wait for 10ns;
    A0 <= '0';
    A1 <= '1';
    A2 <= '0';

    wait for 10ns;
    A0 <= '0';
    A1 <= '1';
    A2 <= '1';

    wait for 10ns;
    A0 <= '1';
    A1 <= '0';

```

```

        A2 <= '0';

        wait for 10ns;
        A0 <= '1';
        A1 <= '0';
        A2 <= '1';

        wait for 10ns;
        A0 <= '1';
        A1 <= '1';
        A2 <= '0';

        wait for 10ns;
        A0 <= '1';
        A1 <= '1';
        A2 <= '1';

    end process;
end Behavioral;

```

2.3 Multiplexer 2 to 16

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY tb2_16 IS
END tb2_16;

ARCHITECTURE behavior OF tb2_16 IS

    COMPONENT mux2_16
    PORT(
        s : IN  std_logic;
        in0 : IN  std_logic_vector(15 downto 0);
        in1 : IN  std_logic_vector(15 downto 0);

```

```

        z : OUT std_logic_vector(15 downto 0)
    );
END COMPONENT;

signal in0 : std_logic_vector(15 downto 0) := (others => '0');
signal in1 : std_logic_vector(15 downto 0) := (others => '0');
signal s : std_logic := '0';

signal z : std_logic_vector(15 downto 0);
-- No clocks detected in port list. Replace <clock> below with
-- appropriate port name

-- constant Clk_period : time := 10 ns;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: mux2_16 PORT MAP (
        in0 => in0,
        in1 => in1,
        s => s,
        z => z
    );

    stim_proc: process
    begin
        wait for 10ns;
        in0 <= x"BEEF";
        in1 <= x"B00B";

        wait for 10ns;
        s <= '1';

        wait for 10ns;
        s <= '0';

        wait for 10ns;
        s <= '1';

    end process;

```

```
END;
```

2.4 Multiplexer 8 to 16

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--USE ieee.numeric_std.ALL;

ENTITY tb8_16 IS
END tb8_16;

ARCHITECTURE behavior OF tb8_16 IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT mux8_16
    PORT(
        s0 : IN  std_logic;
        s1 : IN  std_logic;
        s2 : IN  std_logic;

        in0 : IN  std_logic_vector(15 downto 0);
        in1 : IN  std_logic_vector(15 downto 0);
        in2 : IN  std_logic_vector(15 downto 0);
        in3 : IN  std_logic_vector(15 downto 0);
        in4 : IN  std_logic_vector(15 downto 0);
        in5 : IN  std_logic_vector(15 downto 0);
        in6 : IN  std_logic_vector(15 downto 0);
        in7 : IN  std_logic_vector(15 downto 0);
        z : OUT  std_logic_vector(15 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal in0 : std_logic_vector(15 downto 0) := (others => '0');
    signal in1 : std_logic_vector(15 downto 0) := (others => '0');
```



```

signal in2 : std_logic_vector(15 downto 0) := (others => '0');
signal in3 : std_logic_vector(15 downto 0) := (others => '0');
signal in4 : std_logic_vector(15 downto 0) := (others => '0');
signal in5 : std_logic_vector(15 downto 0) := (others => '0');
signal in6 : std_logic_vector(15 downto 0) := (others => '0');
signal in7 : std_logic_vector(15 downto 0) := (others => '0');

signal s0 : std_logic := '0';
signal s1 : std_logic := '0';
signal s2 : std_logic := '0';

--Outputs
signal z : std_logic_vector(15 downto 0);
-- No clocks detected in port list. Replace <clock> below with
-- appropriate port name

-- constant Clk_period : time := 10 ns;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: mux8_16 PORT MAP (
        in0 => in0,
        in1 => in1,
        in2 => in2,
        in3 => in3,
        in4 => in4,
        in5 => in5,
        in6 => in6,
        in7 => in7,

        s0 => s0,
        s1 => s1,
        s2 => s2,

        z => z
    );

    stim_proc: process
    begin
        wait for 10ns;

```

```

        in0 <= x"BEEF";
        in1 <= x"B00B";
        in2 <= x"BAAA";
        in3 <= x"BABE";
        in4 <= x"FAB0";
        in5 <= x"BADD";
        in6 <= x"DAD3";
        in7 <= x"CA75";

        wait for 10ns;
        s0 <= '0';
        s1 <= '0';
        s2 <= '0';

        wait for 10ns;
        s0 <= '1';
        s1 <= '1';
        s2 <= '1';

        wait for 10ns;
        s0 <= '0';
        s1 <= '0';
        s2 <= '0';

    end process;

END;
```

2.5 Register File

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY tbreg_file IS
END tbreg_file;
```

ARCHITECTURE behavior OF tbreg_file IS

COMPONENT reg_file

PORT(

src_s0 : in std_logic;

src_s1 : in std_logic;

src_s2 : in std_logic;

des_A0 : in std_logic;

des_A1 : in std_logic;

des_A2 : in std_logic;

Clk : in std_logic;

data_src : in std_logic;

data : in std_logic_vector(15 downto 0);

reg0 : out std_logic_vector(15 downto 0);

reg1 : out std_logic_vector(15 downto 0);

reg2 : out std_logic_vector(15 downto 0);

reg3 : out std_logic_vector(15 downto 0);

reg4 : out std_logic_vector(15 downto 0);

reg5 : out std_logic_vector(15 downto 0);

reg6 : out std_logic_vector(15 downto 0);

reg7 : out std_logic_vector(15 downto 0)

);

END COMPONENT;

--Inputs

signal src_s0 : std_logic := '0';

signal src_s1 : std_logic := '0';

signal src_s2 : std_logic := '0';

signal des_A0 : std_logic := '0';

signal des_A1 : std_logic := '0';

signal des_A2 : std_logic := '0';

signal data_src : std_logic := '0';

signal clk : std_logic := '0';

signal data : std_logic_vector(15 downto 0) := (others => '0');

```

--Outputs
signal reg0 : std_logic_vector(15 downto 0);
signal reg1 : std_logic_vector(15 downto 0);
signal reg2 : std_logic_vector(15 downto 0);
signal reg3 : std_logic_vector(15 downto 0);
signal reg4 : std_logic_vector(15 downto 0);
signal reg5 : std_logic_vector(15 downto 0);
signal reg6 : std_logic_vector(15 downto 0);
signal reg7 : std_logic_vector(15 downto 0);

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: reg_file PORT MAP (
        src_s0 => src_s0,
        src_s1 => src_s1,
        src_s2 => src_s2,

        des_A0 => des_A0,
        des_A1 => des_A1,
        des_A2 => des_A2,

        data_src => data_src,
        Clk => clk,
        data => data,

        reg0 => reg0,
        reg1 => reg1,
        reg2 => reg2,
        reg3 => reg3,
        reg4 => reg4,
        reg5 => reg5,
        reg6 => reg6,
        reg7 => reg7

    );

    -- Clock process definitions
    clk_process :process
begin

```

```

        clk <= '0';
        wait for 5ns;
        clk <= '1';
        wait for 5ns;
end process;

-- Stimulus process
stim_proc: process
begin
    wait for 10ns;
    des_a0 <= '0';
    des_a1 <= '0';
    des_a2 <= '0';
    data <= x"0000";

    wait for 10ns;
    des_a0 <= '0';
    des_a1 <= '0';
    des_a2 <= '1';
    data <= x"1111";

    wait for 10ns;
    des_a0 <= '0';
    des_a1 <= '1';
    des_a2 <= '0';
    data <= x"2222";

    wait for 10ns;
    des_a0 <= '0';
    des_a1 <= '1';
    des_a2 <= '1';
    data <= x"3333";

    wait for 10ns;
    des_a0 <= '1';
    des_a1 <= '0';
    des_a2 <= '0';
    data <= x"4444";

    wait for 10ns;
    des_a0 <= '1';

```

```

        des_a1 <= '0';
        des_a2 <= '1';
        data <= x"5555";

        wait for 10ns;
        des_a0 <= '1';
        des_a1 <= '1';
        des_a2 <= '0';
        data <= x"6666";

        wait for 10ns;
        des_a0 <= '1';
        des_a1 <= '1';
        des_a2 <= '1';
        data <= x"7777";


    end process;

END;


```

3 Testbench Results


3.1 Register

 


3.2 Decoder

 

3.3 2-16 Multiplexer

 

3.4 8-16 Multiplexer

 

3.5 Register File

